

4.1 基本触发器的逻辑符号与输入波形如图P4.1所示。试作出 Q 、 $\bar{Q}$ 的波形。

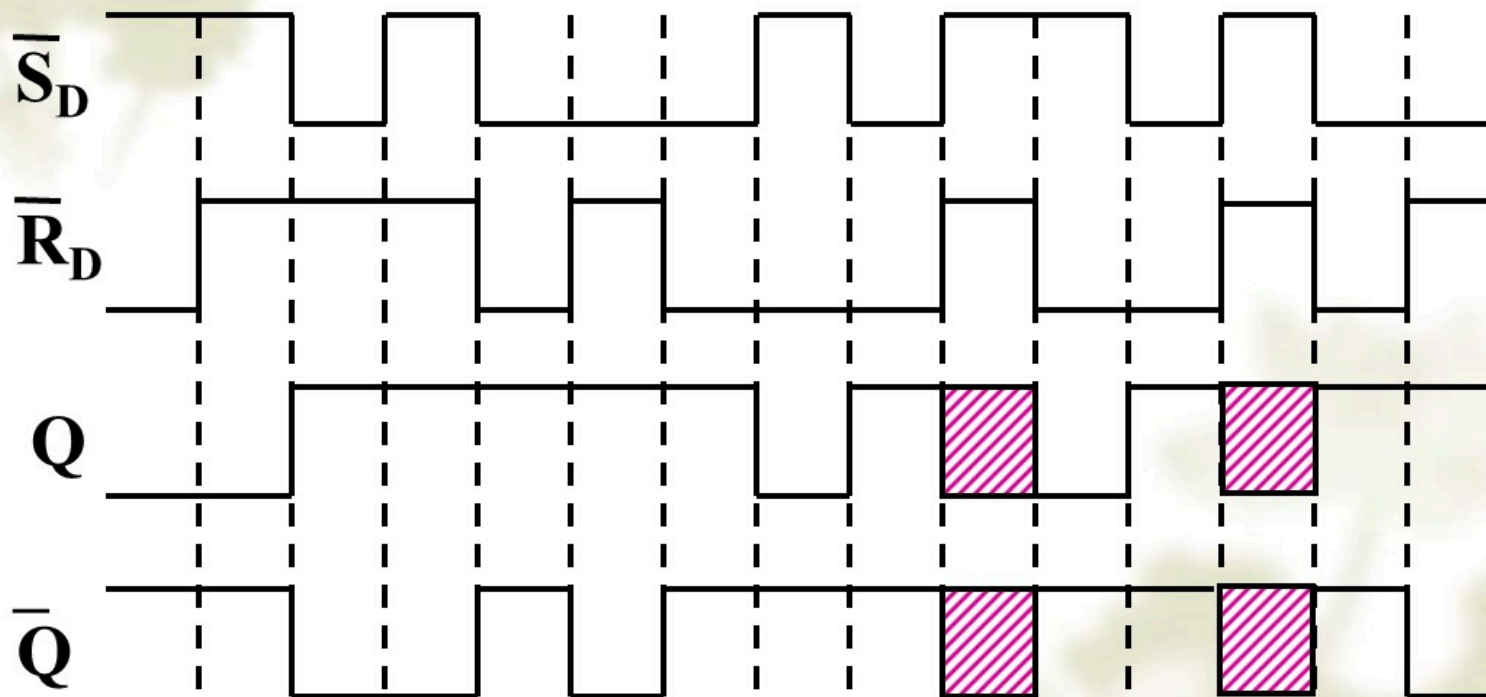


图 P5.1

4.3 对于图P4.3电路,试导出其特征方程并说明对A、B的取值有无约束条件。

解: (1)列功能表

A	B	Q^{n+1}
0	0	1
0	1	1
1	0	Q^n
1	1	1

(2) 特征方程

		BQ^n			
		00	01	11	10
A	0	1	1	1	1
	1	0	1	1	1

$$Q^{n+1} = \bar{A} + B + Q^n$$

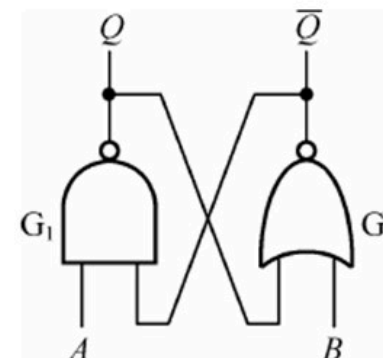


图 P4.3

(3) 对A、B的取值无约束条件。

4.4试写出图 P4.4 触发器电路的特征方程。

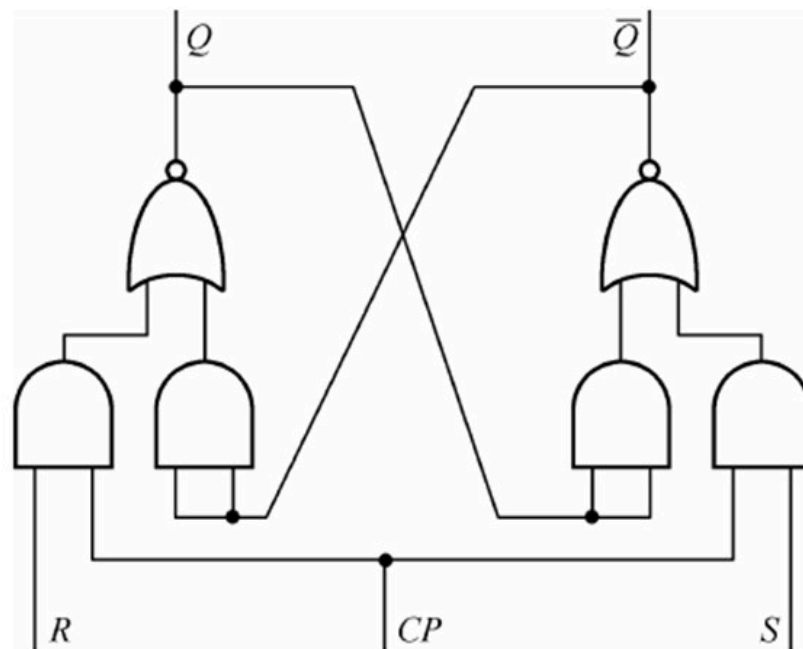


图 P4.4


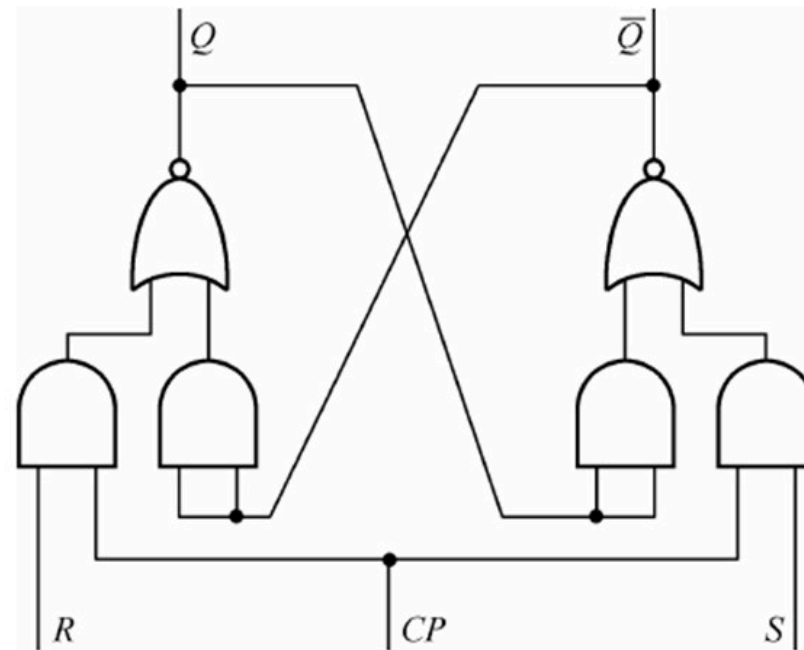


图 P4.4


CP=0时, $Q^{n+1}=Q^n$

CP=1时, $\begin{cases} Q^{n+1}=S+\bar{R}Q^n \\ SR=0 \end{cases}$


4.5 试写出图 P4.5 各触发器的次态方程。

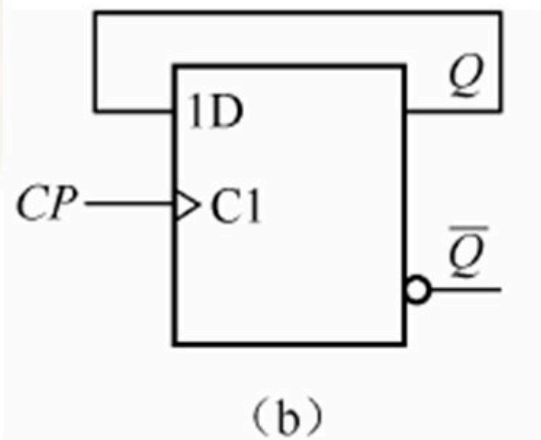
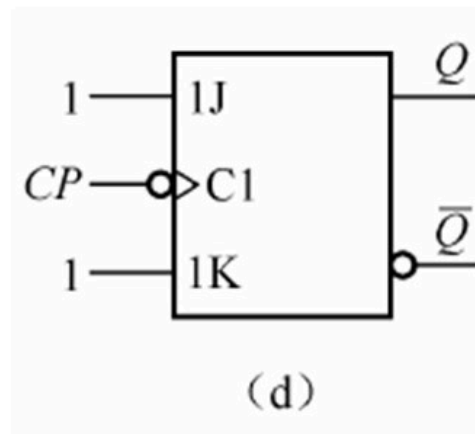
$$\begin{aligned} Q^{n+1} &= D \cdot CP \uparrow \\ &= [Q^n] \cdot CP \uparrow \end{aligned}$$



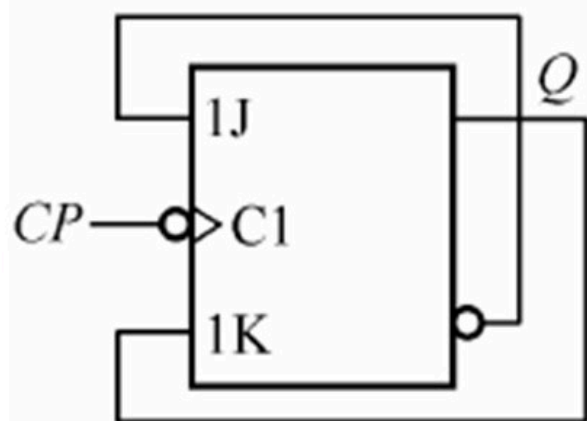
$$\begin{aligned} Q^{n+1} &= [J\bar{Q}^n + \bar{K}Q^n] CP \downarrow \\ &= [1\bar{Q}^n + \bar{1}Q^n] CP \downarrow \\ &= [\bar{Q}^n] CP \downarrow \end{aligned}$$



(e)

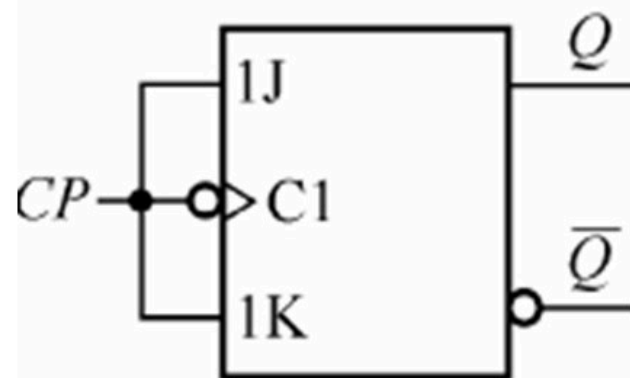
$$\begin{aligned}
 Q^{n+1} &= [J\overline{Q}^n + \overline{K}Q^n]CP \downarrow \\
 &= [\overline{Q}^n\overline{Q}^n + \overline{Q}^nQ^n]CP \downarrow \\
 &= [\overline{Q}^n]CP \downarrow
 \end{aligned}$$



(g)

$$\begin{aligned}
 Q^{n+1} &= [J\overline{Q}^n + \overline{K}Q^n]CP \downarrow \\
 &= [CP\overline{Q}^n + \overline{CP}Q^n]CP \downarrow \\
 &= [1\overline{Q}^n + \overline{1}Q^n]CP \downarrow \\
 &= [\overline{Q}^n]CP \downarrow
 \end{aligned}$$

4.8画出图P4.8中Q端的波形。设初态为“0”。

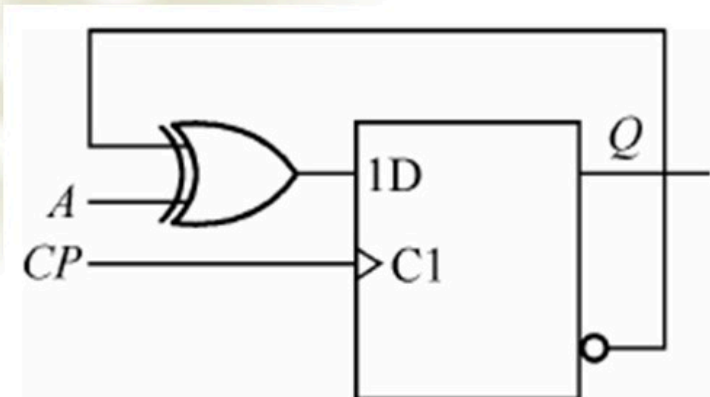

解：特征方程为：

$$Q^{n+1} = D \cdot CP \uparrow \\ = [\bar{Q}^n \oplus A] \cdot CP \uparrow$$

A=0时，翻转；
A=1时，保持。

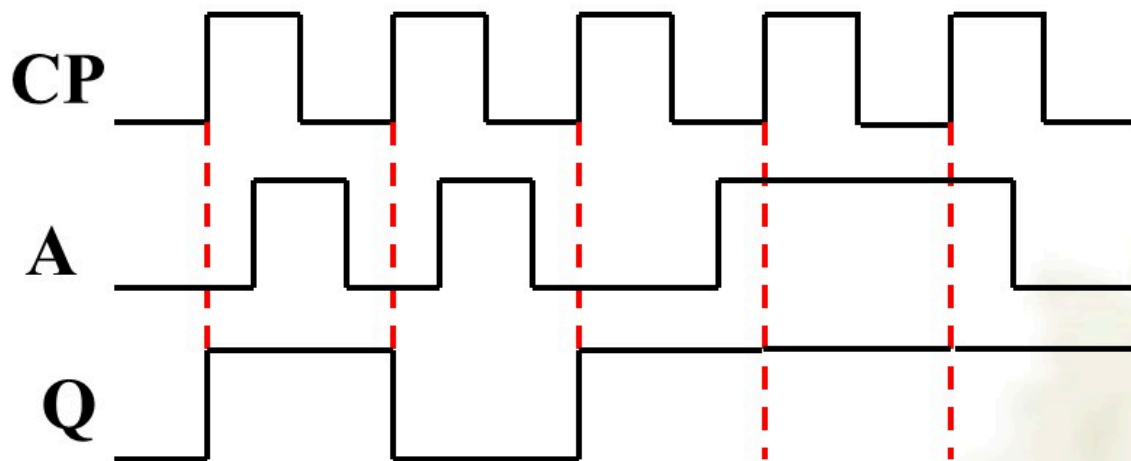


图 4.8

4.11 画出图P4.11电路中 Q_1 和 Q_2 的波形。

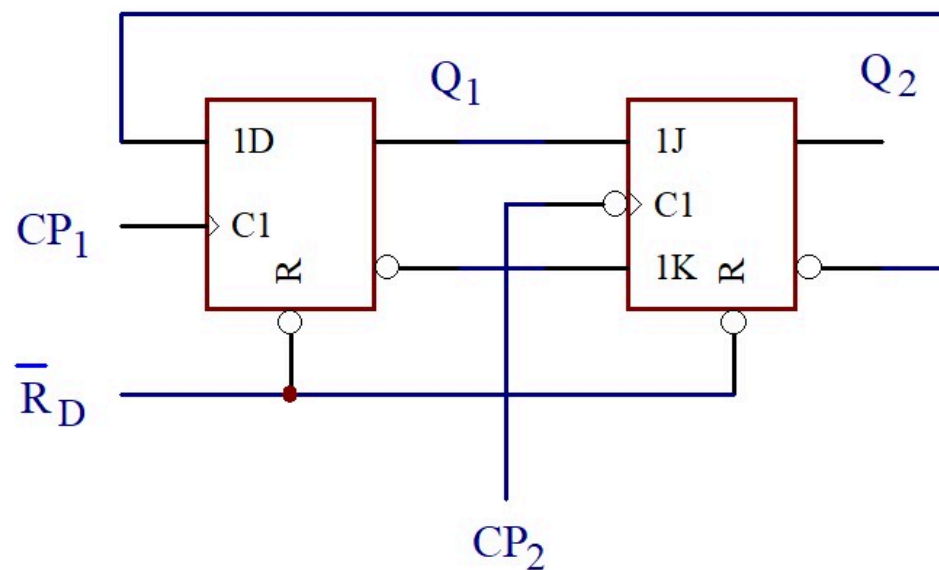



图 4.11

解：特征方程为：


$$Q_1^{n+1} = [\bar{Q}_2^n] CP_1 \uparrow$$

$$Q_2^{n+1} = [Q_1^n] CP_2 \downarrow$$
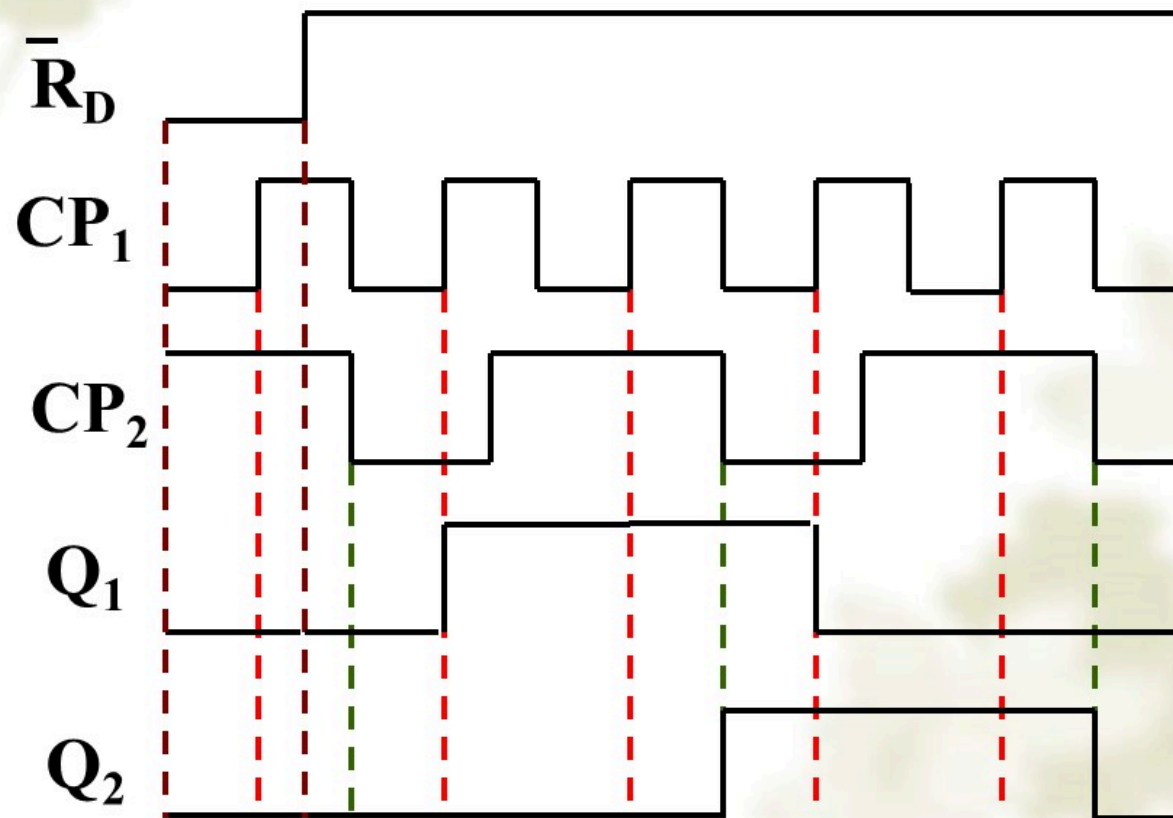
$$Q_1^{n+1} = [\bar{Q}_2^n]CP_1\uparrow \quad Q_2^{n+1} = [Q_1^n]CP_2\downarrow$$



4.17 试作出图P4.17电路中 Q_1 、 Q_2 的波形。

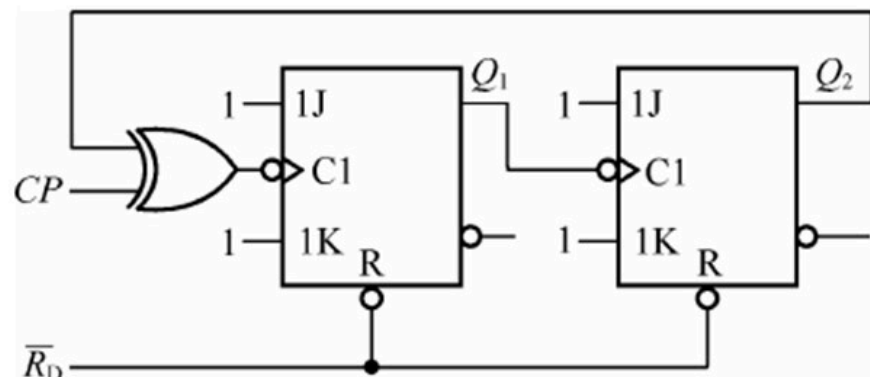

$Q_2=0$ 时

$$Q_1^{n+1} = [\bar{Q}_1^n] \cdot (CP \oplus Q_2) \downarrow$$

$$\begin{aligned} Q_1^{n+1} &= [Q_1^n] \downarrow (CP \oplus 0) \downarrow \\ &= [Q_1^n] \downarrow (CP) \downarrow \end{aligned}$$

$Q_2=1$ 时


$$Q_1^{n+1} = [Q_1^n] \downarrow (CP \oplus 1) \downarrow$$

$$= [Q_1^n] \downarrow (\overline{CP}) \downarrow$$

$$= [Q_1^n] \downarrow (CP) \uparrow$$

10

4.17 试作出图P4.17电路中 Q_1 、 Q_2 的波形。

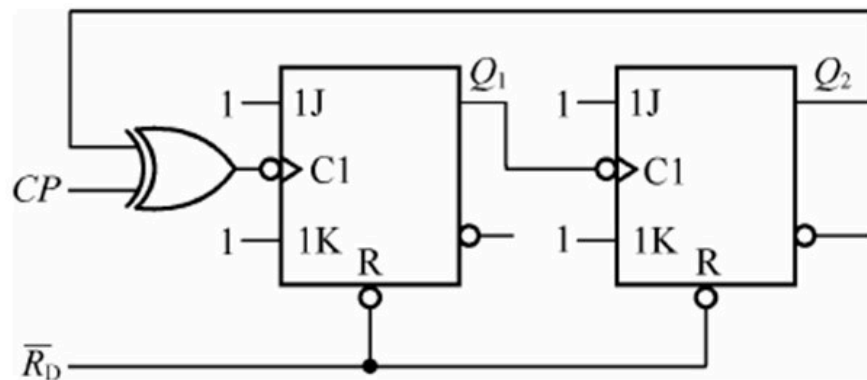


$$Q_1^{n+1} = [\bar{Q}_1^n] \cdot (CP \oplus Q_2) \downarrow$$


$Q_2=0$ 时, $CP \downarrow$

$Q_2=1$ 时, $CP \uparrow$

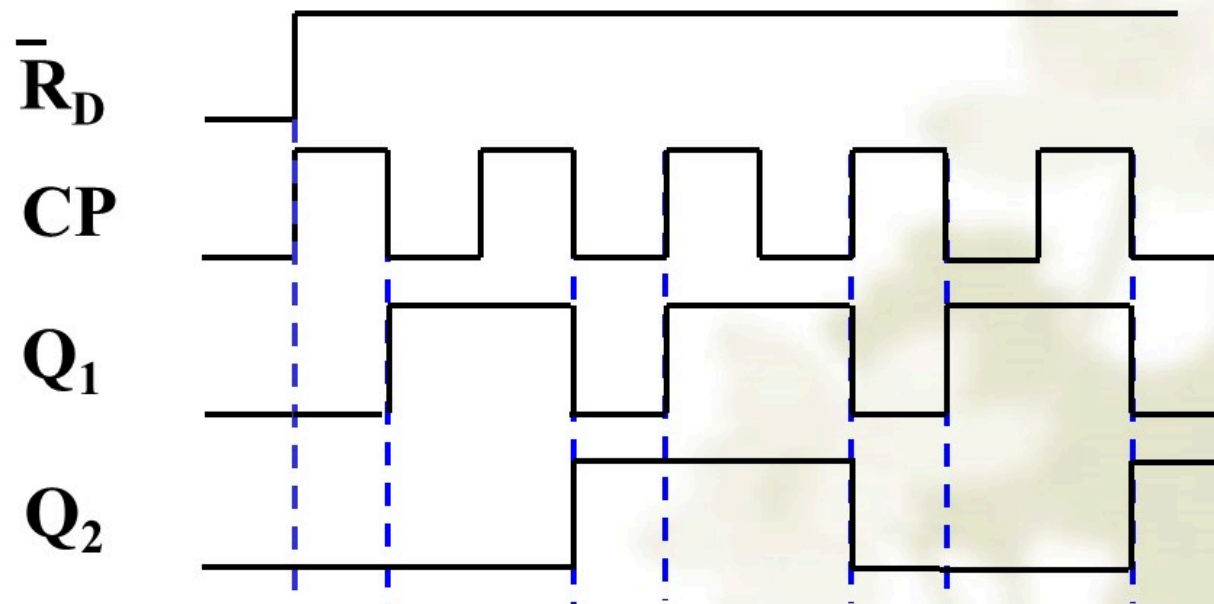
$$Q_2^{n+1} = [\bar{Q}_2^n] \cdot Q_1 \downarrow$$



4.19 已知电路如图P4.19，试作出Q端的波形。设Q的初态为“0”。

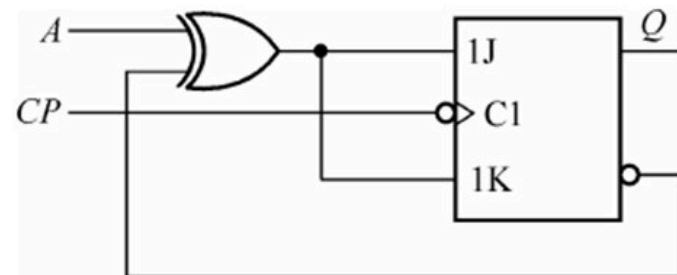
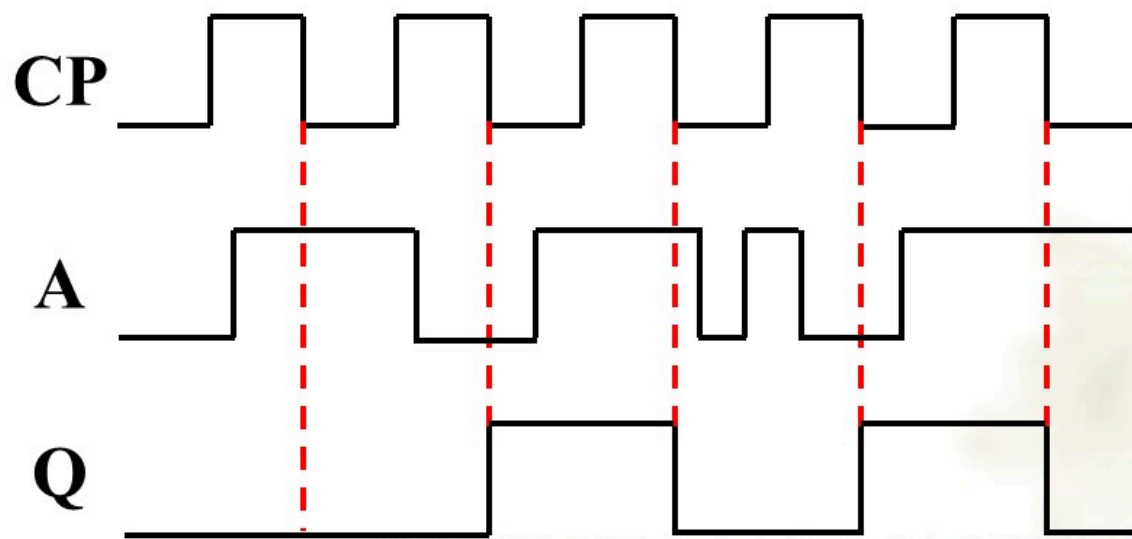
$$\begin{aligned}
 Q^{n+1} &= [J\bar{Q}^n + \bar{K}Q^n] CP \downarrow \\
 &= \left[(A \oplus \bar{Q}^n) \bar{Q}^n + (\overline{A \oplus \bar{Q}^n}) Q^n \right] CP \downarrow \\
 &= [\bar{A}] CP \downarrow
 \end{aligned}$$



12